



Visions for On-Chip Integrated Distributed Amplifier & Antenna Systems in SiGe BiCMOS for Ultra Large Bandwidth

F. Ellinger, D. Fritsche, J.D. Leufker,

M. Laabs and D. Plettemeier

Technische Universität Dresden



I feel the need the need for speed

Tom Mitchel (Tom Cruise),

Movie Top Gun



Outline

How can we get in SiGe BiCMOS technology:

- Ultra high operation frequencies
- Ultra high bandwidths
- High gain
- High output power



Operation at ultra-high frequencies

- Very fast and scaled transistors

⇒ Low V_{dc} & signal power

- High air-channel losses

⇒ Optimization of PAs challenging but very important

$$P_{PA} \sim V_{dc}^2 / Z_L$$


⇒ Very low Z_L for high TX power

⇒ Large impedance transformation



⇒ High losses

Transformer Based Power Adding

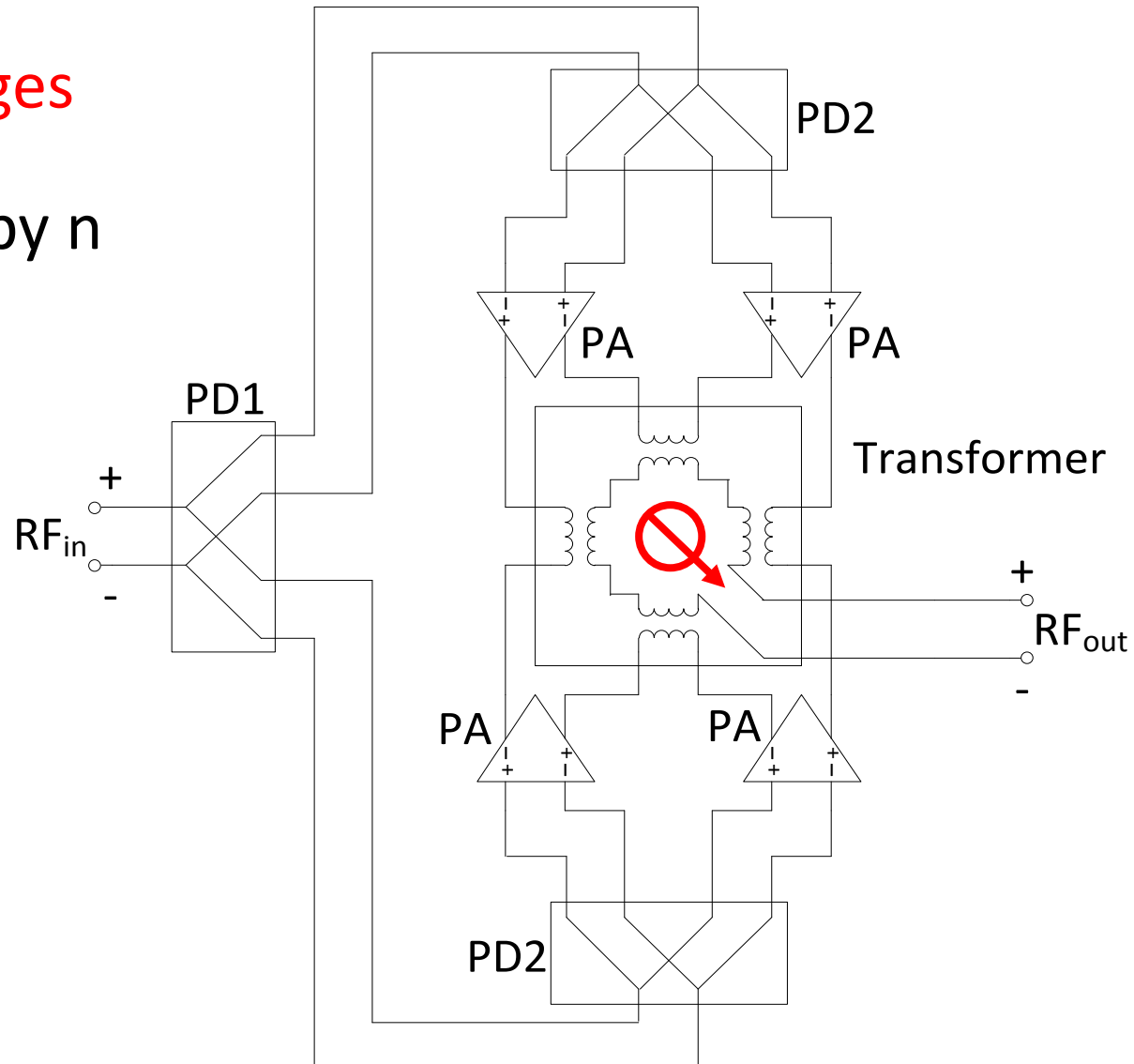- Adding of n ac voltages
- TX power increases by n
- Required $Z_L \uparrow$ by n
- Z-trafo smaller
- Higher efficiency
- Larger BW




Combining PA at 60 GHz in SiGe

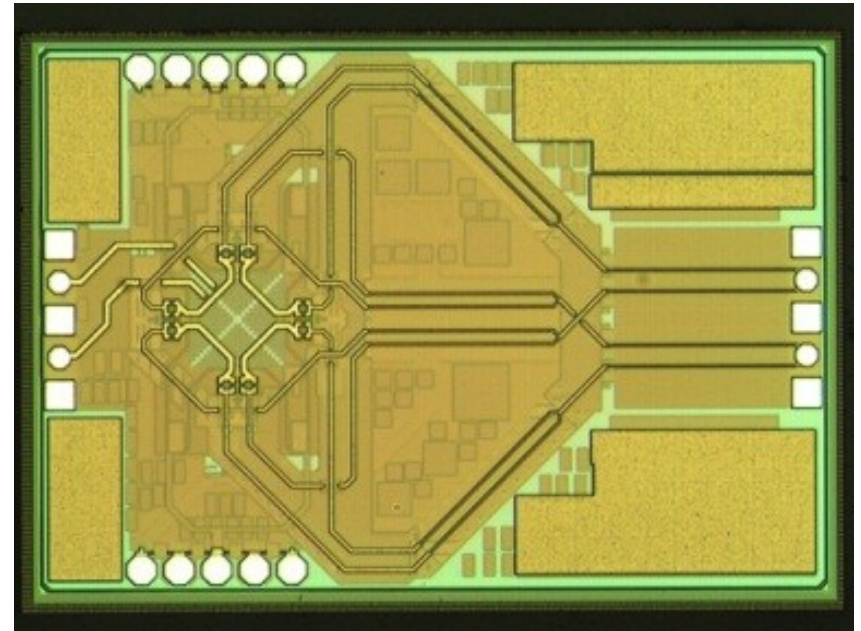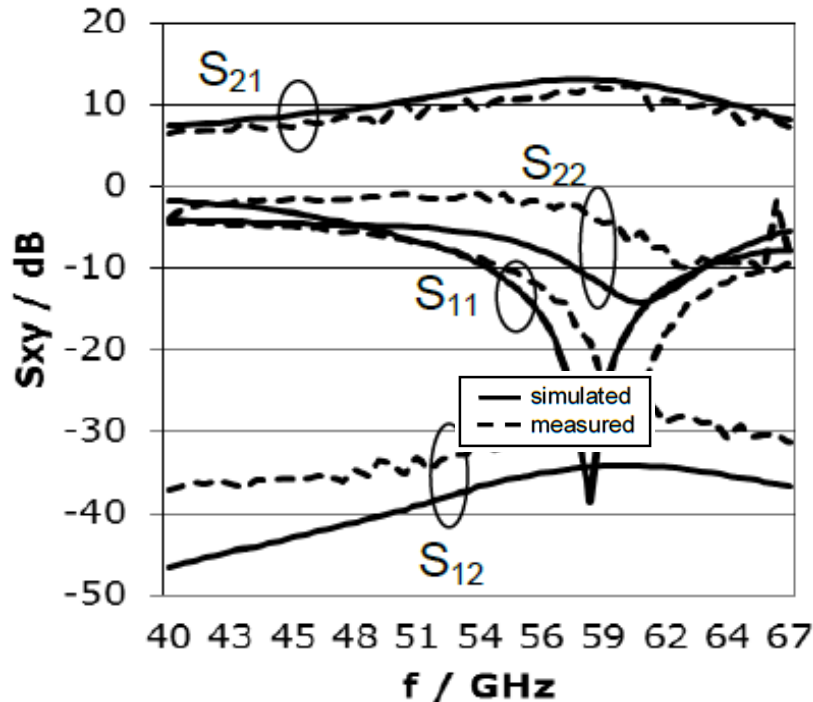


Ref.	f/BW [GHz]	P_{1dB} [dBm]	PAE [%] @ P_{1dB} /peak	V_{dc} [V]	Technology
TUD	60/12	23.5	> 13	3.3	0.25 μm SiGe
[Pfe07]	62	21	n.a./6.3	4	0.13 μm SiGe
[Wan12]	79	16.4	13/19.2	1	65 nm CMOS
[Dea08]	270	7.7	4/n.a.	1.7	35 nm InP HEMT

160-210 GHz SiGe LNA

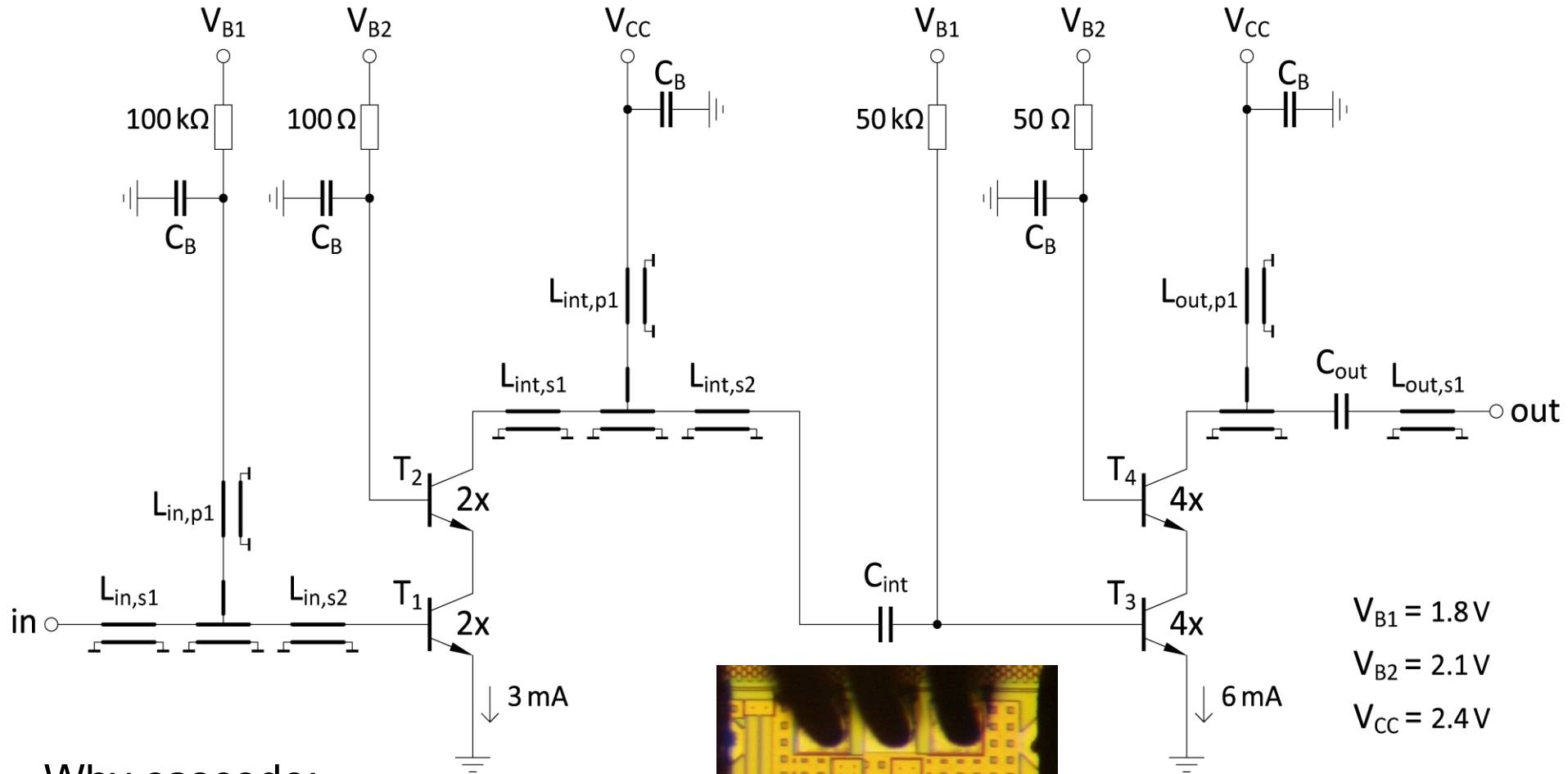


Why cascode:

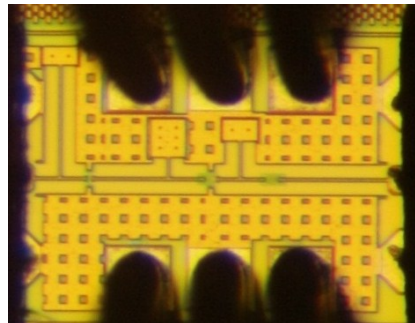- High Rout → high gain
- Low Miller effect → high f





Measurements

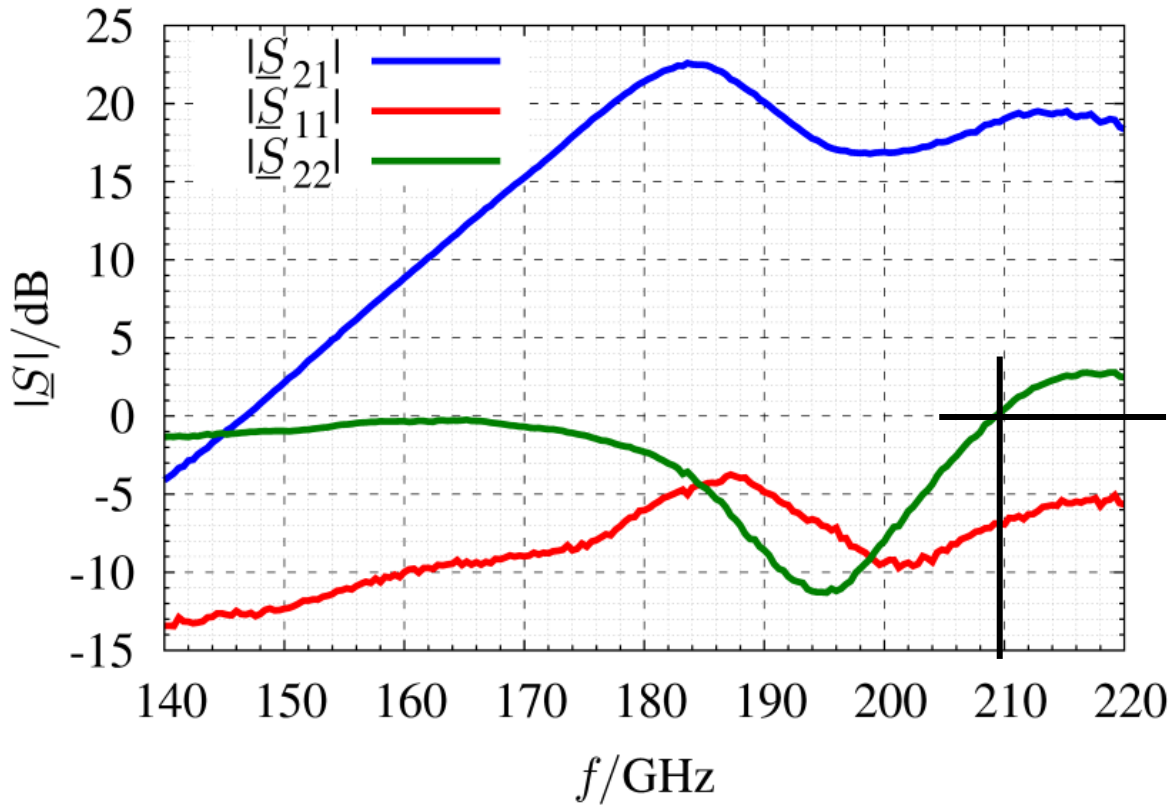


$S_{22} > 0$ dB at $f > 210$ GHz

Redesign with $S_{22} < 0$
in fabrication

Ref.	Technology	f/GHz	BW/GHz	G/dB	P_{DC} /mW	A/mm ²
TUD	130 nm SiGe HBT	205	> 30 (50)	17	22	0.24
[Tess09]	50 nm GaAs mHEMT	200	40	16	24	1.0
[Sch12]	130 nm SiGe HBT	245	10	18	303	0.15




Higher Cascode MAG by L_{peaking}

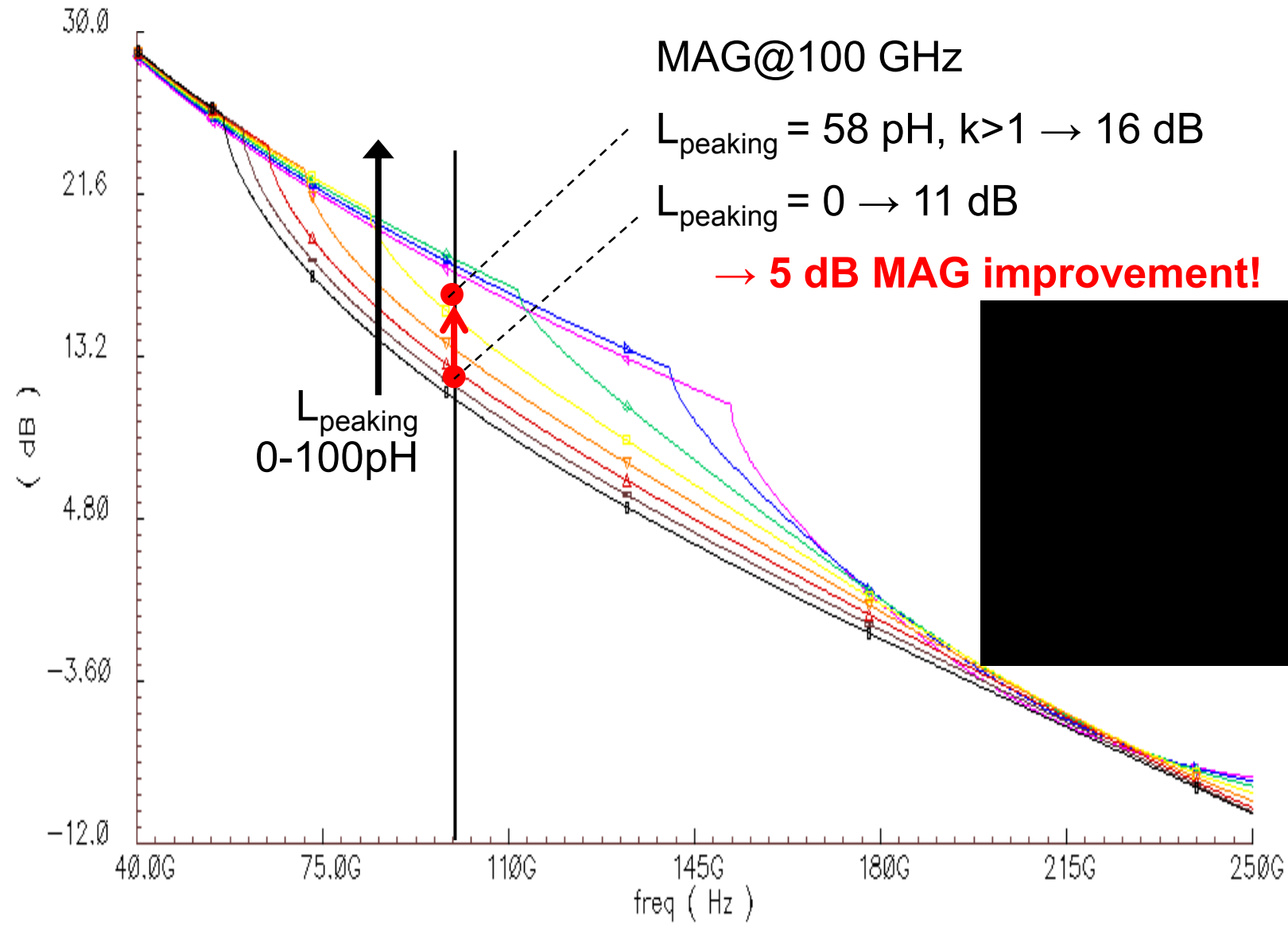



BW Limited by Parasitic Capacitances Generating Lowpass Filter

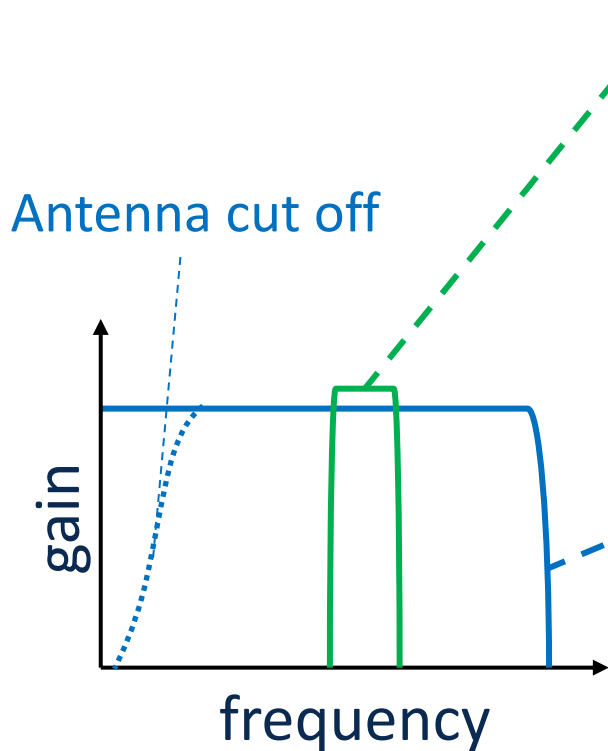

Method 1:

Resonate capacitances with inductors

⇒ Narrowband impedance matching

⇒ Low bandwidth

Method 2:

Incorporate capacitances into active equivalent transmission lines


⇒ Distributed (traveling wave) LC structure

⇒ Wideband impedance matching

⇒ High bandwidth




Traveling Wave Amplifier

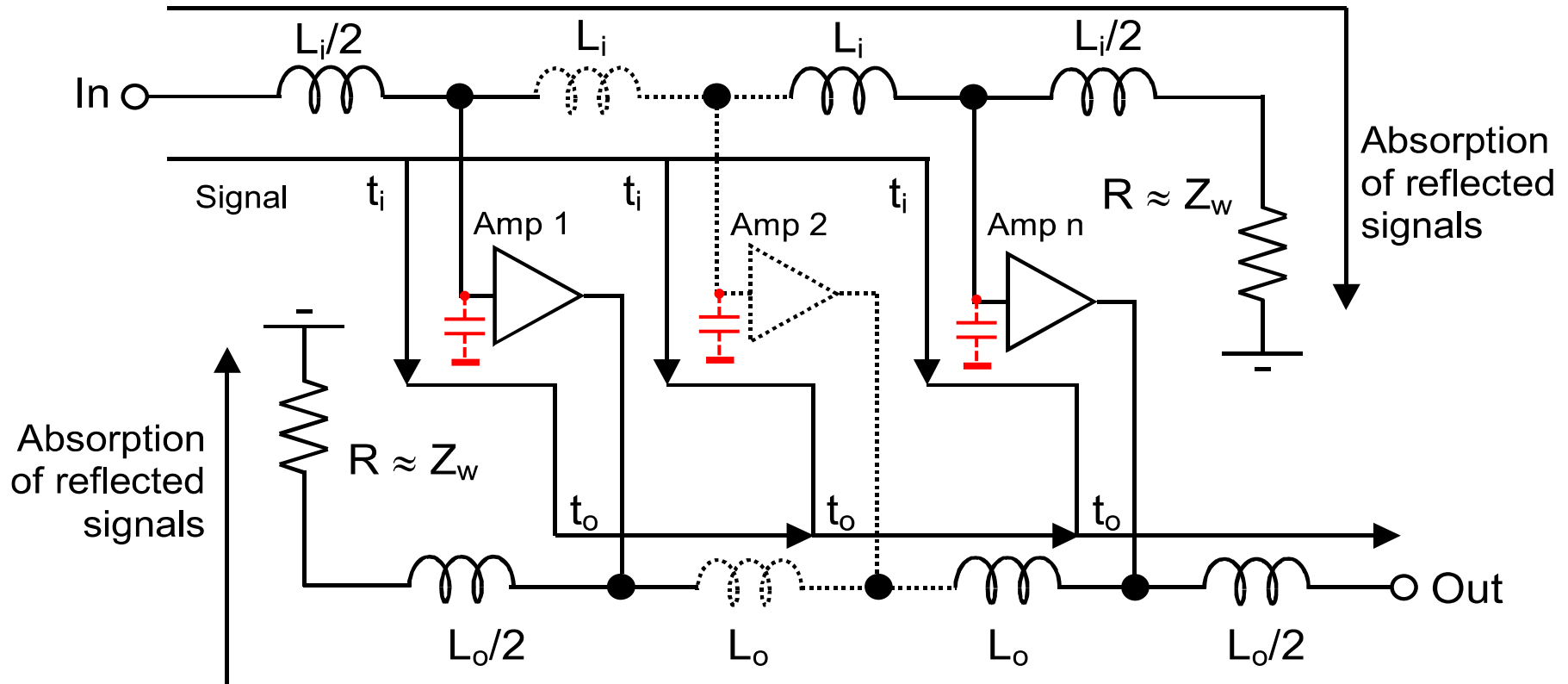



Cascaded TWA

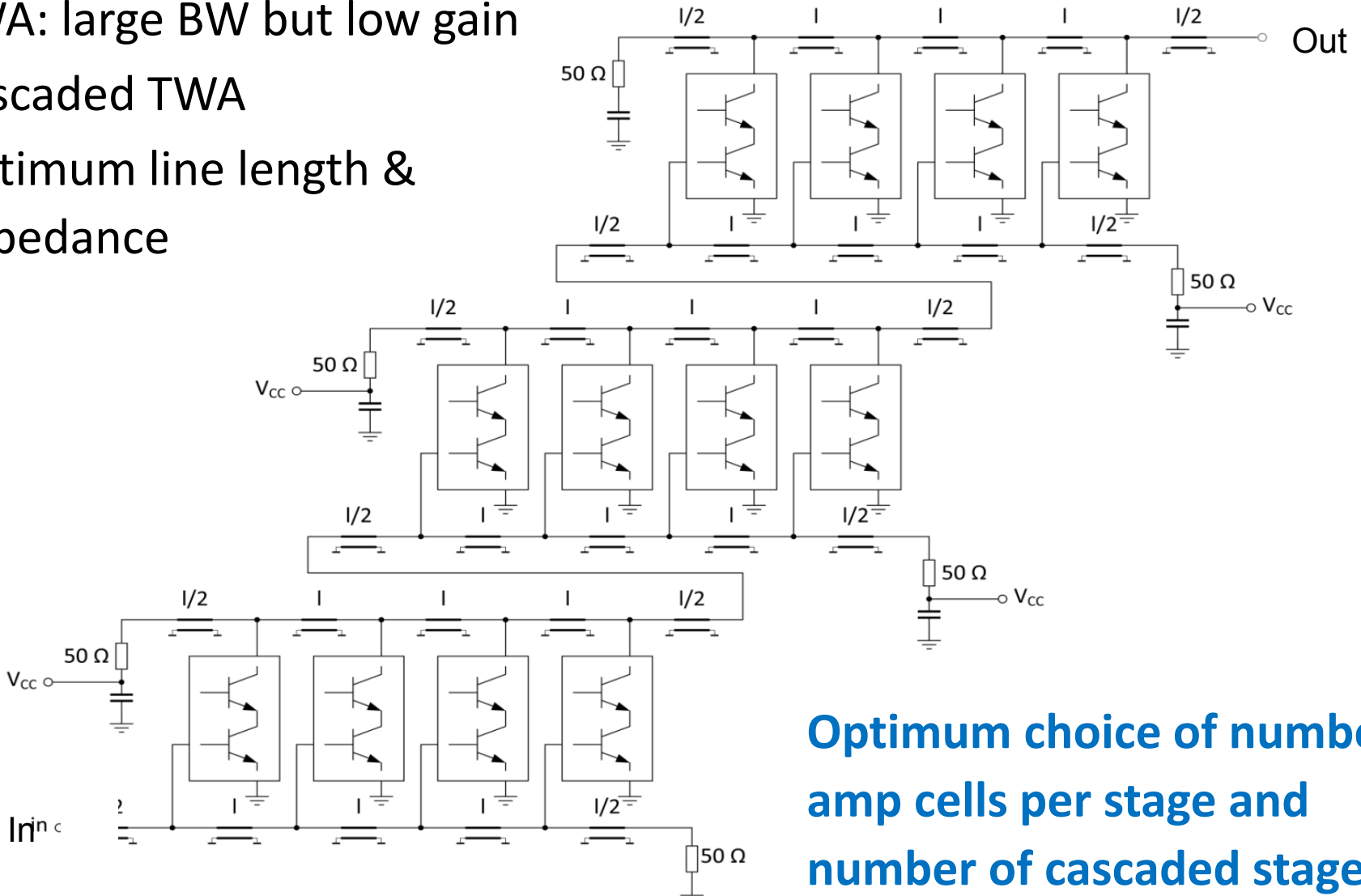
- TWA: large BW but low gain
- Cascaded TWA
- Optimum line length & impedance



**Optimum choice of number
amp cells per stage and
number of cascaded stages**



Simulations Results, IC in FAB

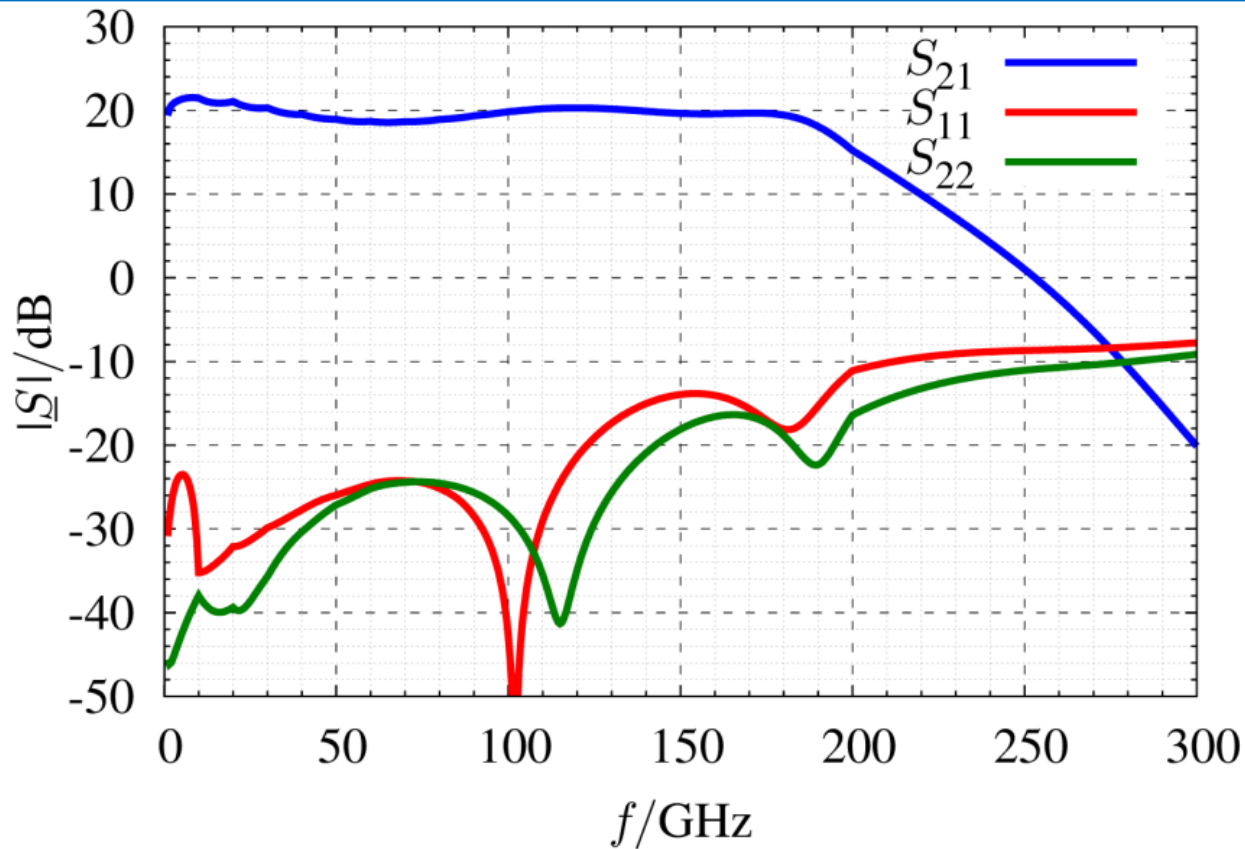

Reference	Technology	Gain/dB	BW/GHz	P_{DC} /mW	A/mm ²
Group Ellinger, sim.	130 nm SiGe	20	190	200	0.6
Niknejad, RFIC12	130 nm SiGe	24	110	248	0.65
Zech, GeMiC12	50 nm GaAs HEMT	11	110	450	1.7



Vision of DAAB Project: Subproject within DFG SPP 100 Gb/s & Beyond

- Integration of antennas and amplifiers on single chip
 - Lower connection losses, 50Ω matching not needed, peaking
- State of the art for antenna & amplifier frontend on single chip:
 - GaAs HEMT: BW = 30 @ 220 GHz → 14 %, Gunnarson MWCL 08
 - SiGe HBT: BW = 15 @ 170 GHz → 9 %, Laskin RFIC 08


Narrowband resonant matching

- Relative frontend BW of up to 50 % (e.g. 150-250 GHz)
- Novel fully distributed antenna & amplifier systems



Approach 1: Wideband TWA & Antenna on Single Chip

- ⇒ Large BW
- ⇒ Relative low risk
- ⇒ Benchmark approach

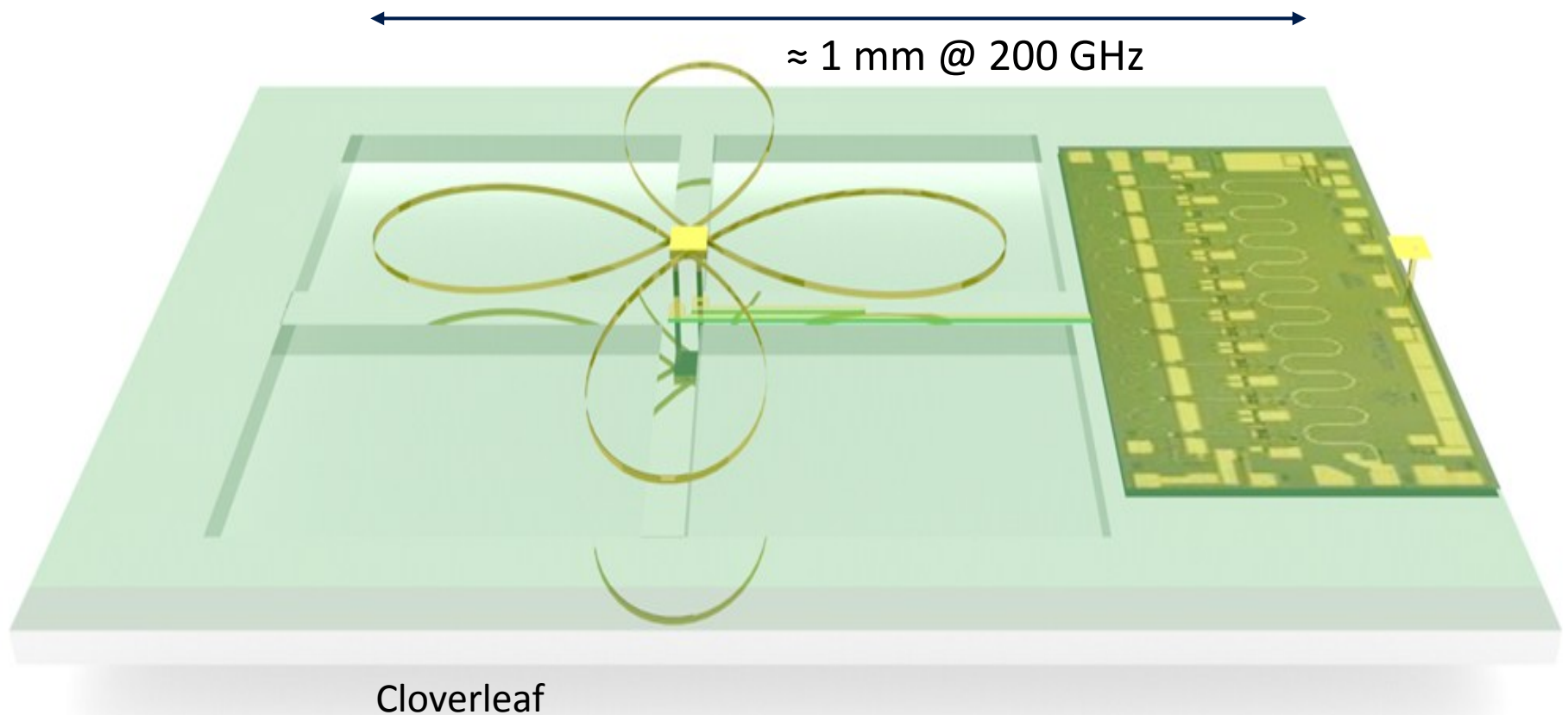




Approach 2: Antennas at Different Metal Levels & Locations and Multiple TWAs

Very large BW

⇒ More signal radiated upwards and lower substrate losses

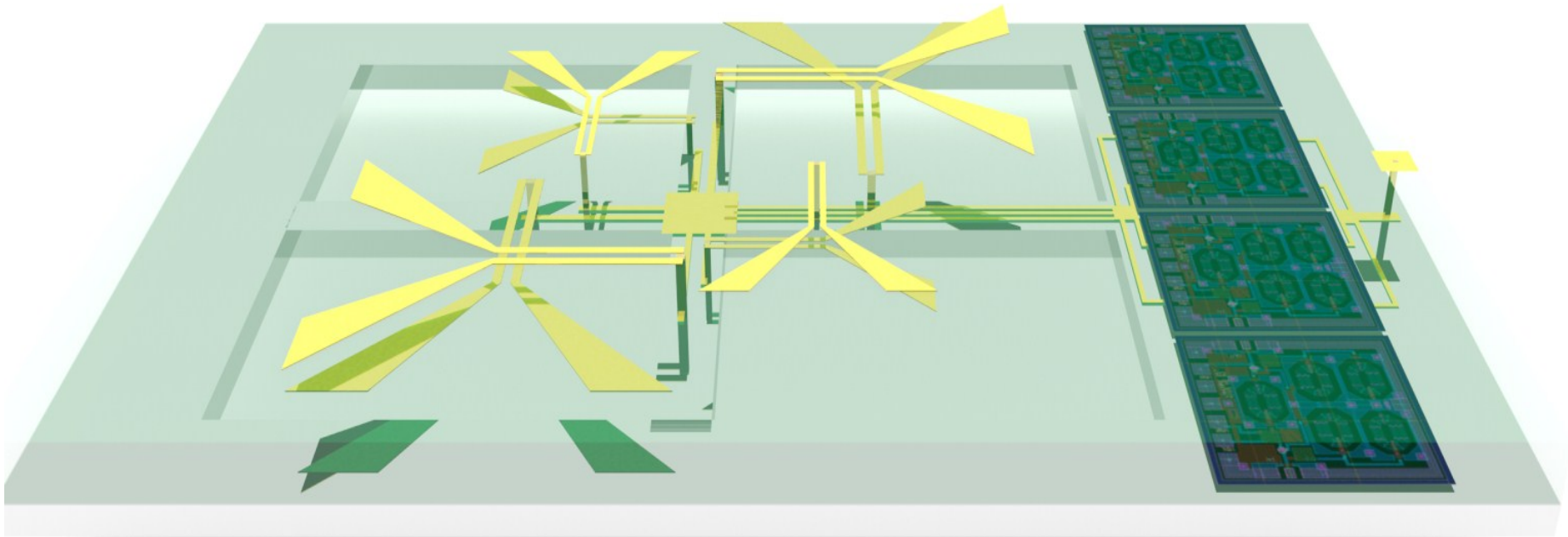Substrate etching lowers losses especially at lower metal levels




Linear tapered slot



Approach 3: Multiple Antenna Contact Points and Multiple Frequency Scaled Amps

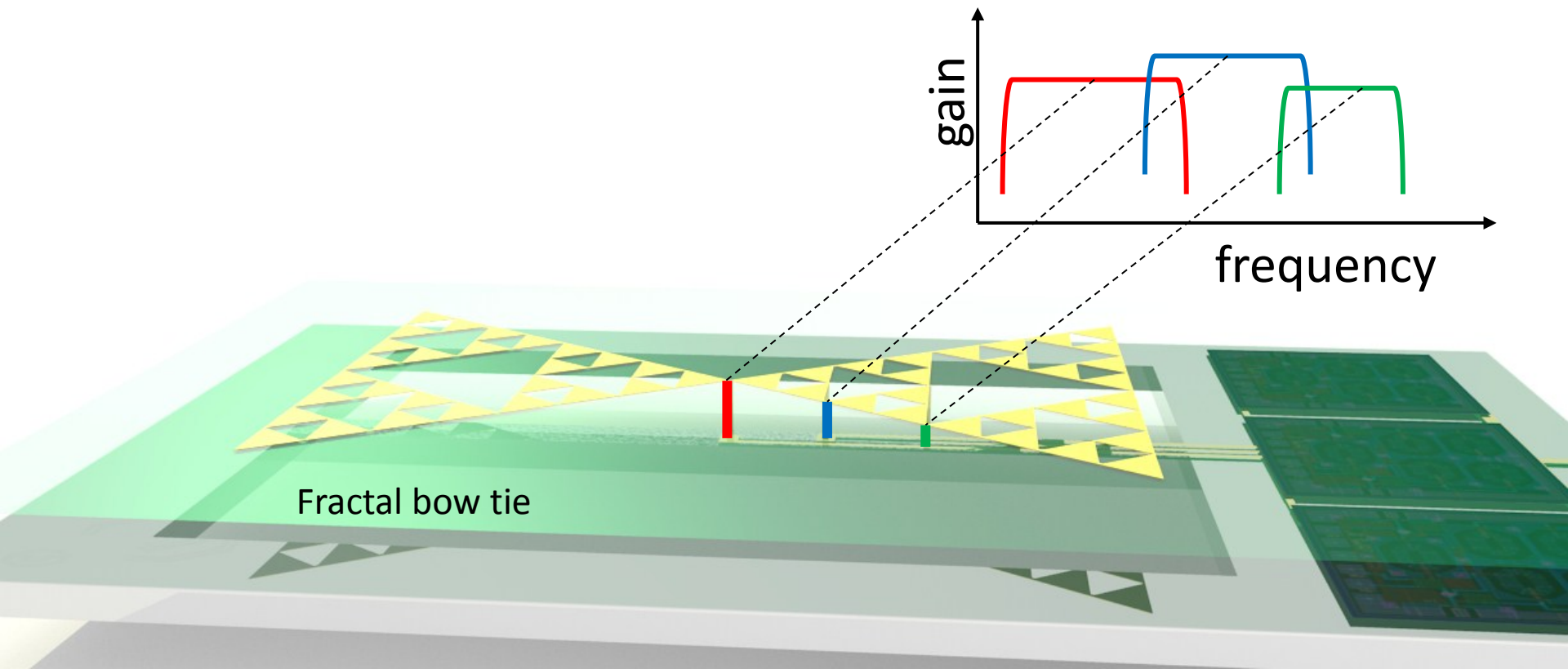
- ⇒ Different contact points have different optimum centre frequencies
- ⇒ Adding of multiple bands by frequency scaled amplifiers
- ⇒ Very large BW






Antenna Losses in Dependency of Field and Port Position

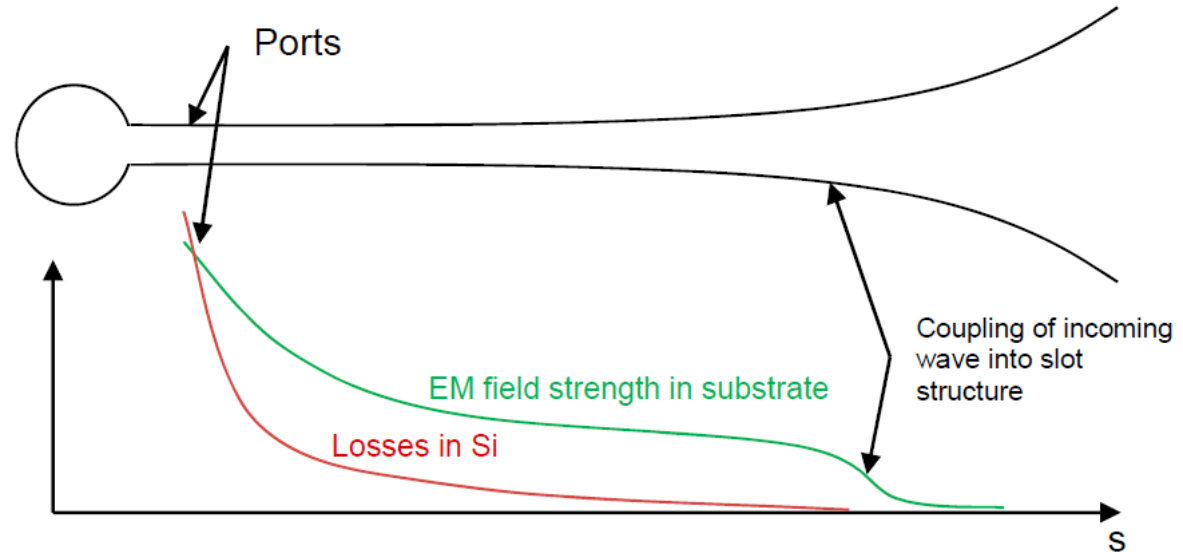Conventional: Whole energy via single point
⇒ losses \sim amplitude²
⇒ large substrate losses



Distributed: energy fed via several points
⇒ lower losses

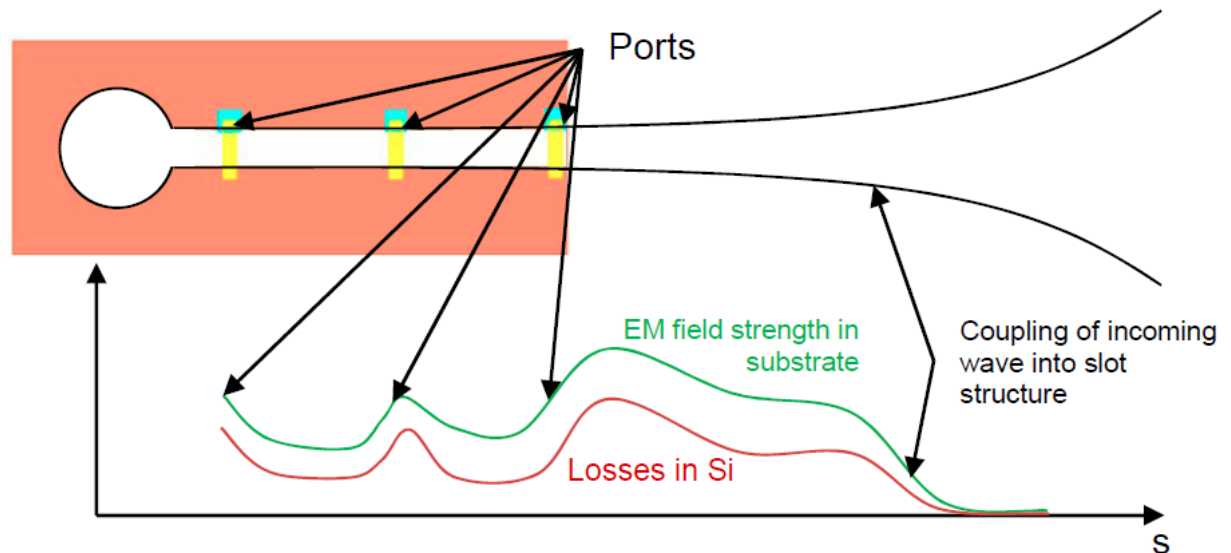




Approach 4: Multiple Antenna Contact Points & Distributed Adding with one TWA

Antenna feeding points as transmission line elements for amplifier
towards fully distributed system

⇒ Higher BW

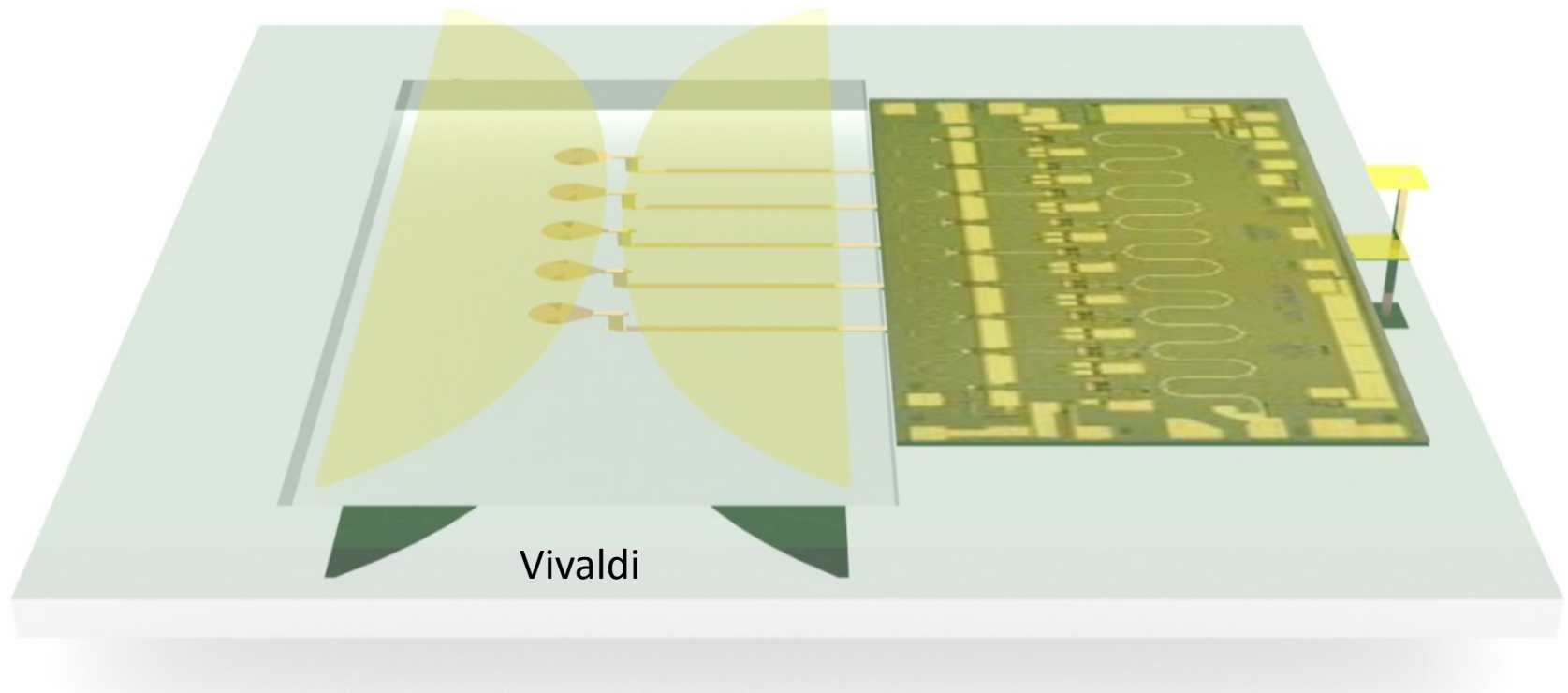



Summary

- **SiGe ICs**

- 160-210 GHz 22 mW amplifier
- TWA with 190 GHz BW
- 60 GHz PA with 23.5 dBm Pout

- **Visions for broadband amp & antenna frontends at 150-250 GHz**

- Several metal layers to minimize fields penetrating substrate
- Combined antennas with different feeding points = center freq.
- Fully distributed systems: antenna feeding points part of amp



Acknowledgements, Funding

- DFG SFB HAEC
- DFG SPP 100 Gb/s and Beyond



**Dresden University of Technology
thanks you for your attention!**



Frank.Ellinger@tu-dresden.de